


Topics to be Discussed

- **Series *RL* Circuit.**
- **How to Draw Phasor Diagram.**
- **Complex Impedance.**
- **Impedance Triangle.**
- **Series *RC* Circuit.**
- **Complex Power.**
- **Series *RLC* Circuit.**

Next



Series *RL* Circuit

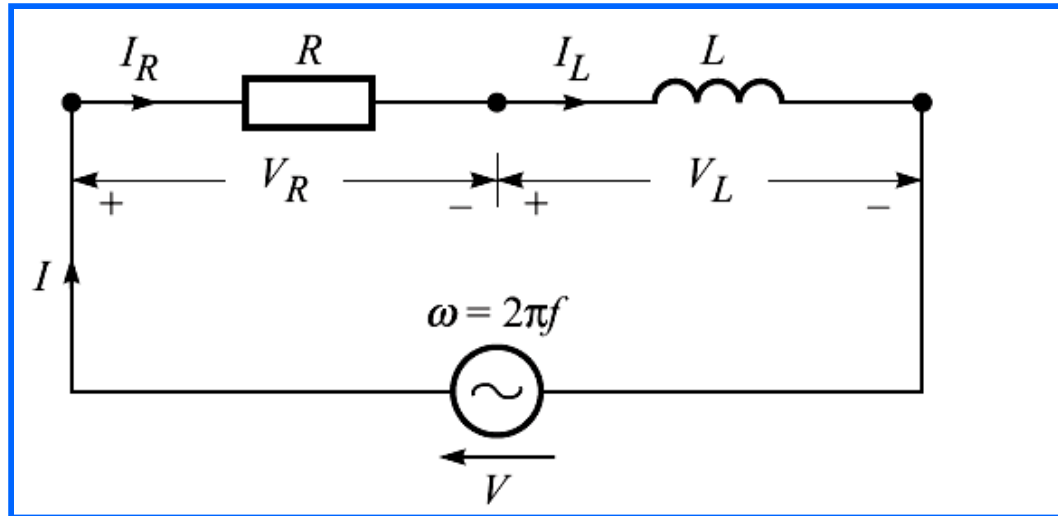

To write $V = V_R + V_L$ is **wrong**.

In AC circuits, the two voltages must be added by treating them as *phasors*,

$$\mathbf{V} = \mathbf{V}_R + \mathbf{V}_L$$

Next




How to Draw Phasor Diagram

1. Mark the source voltage V , with its polarity. Mark the source current I leaving the positive terminal.
2. Mark 'the voltage across' and 'the current through' each individual component of the circuit, following the [passive sign convention](#).
3. Draw the phasor diagrams for individual components.
4. Superimpose all the individual phasor diagrams, by recognizing the *common phasor* among them.
5. For this, you may have to rotate some phasor diagrams.
6. Find the phasor addition by drawing the parallelogram.


Next



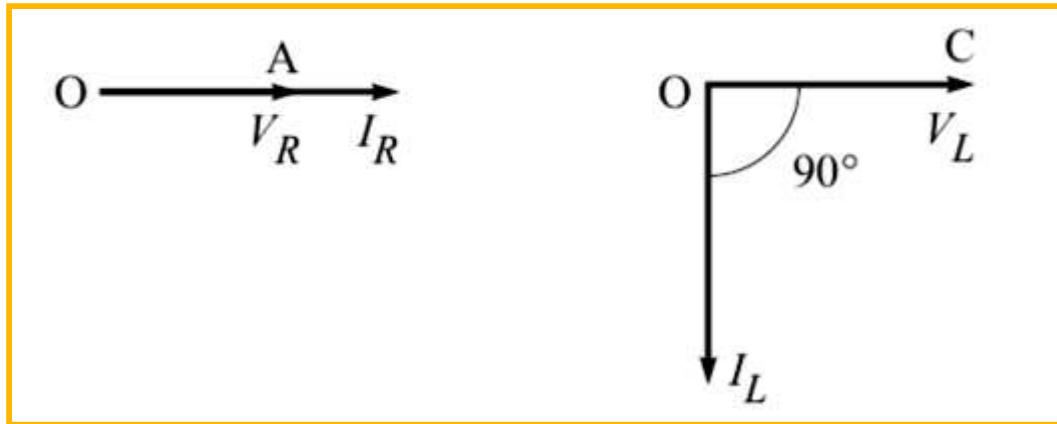

(b) Phasor diagram for R .

(c) Phasor diagram for L .

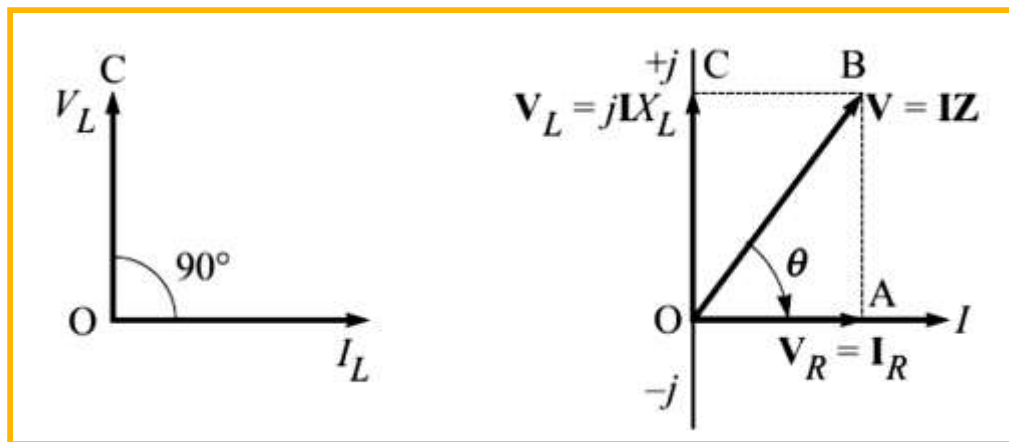

(d) Phasor diagram for L , rotated by $+90^\circ$.

(e) The complete phasor diagram.

Next



Complex Impedance

Complex impedance

$$= R + jX \qquad = (\text{resistance}) + j (\text{reactance}) \qquad \text{or} \qquad \mathbf{Z}$$


For the series RL circuit,

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = R + j\omega L = Z \angle \theta$$

$$\text{where, } Z = \sqrt{R^2 + (\omega L)^2} \quad \text{and} \quad \theta = \tan^{-1} \frac{\omega L}{R}$$

Next 

Impedance Triangle

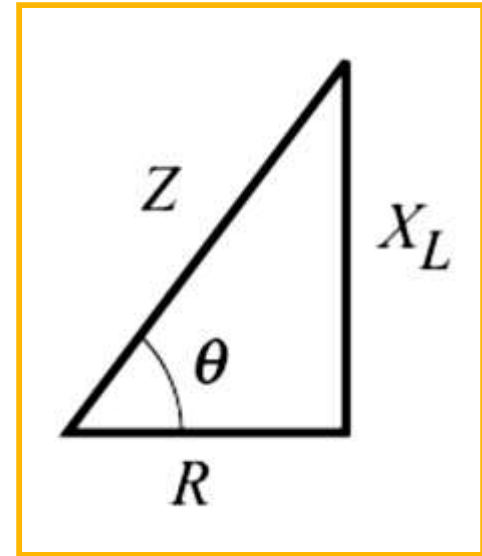

- We can separate the voltage triangle OAB.
- Dividing each side of this triangle by I , we get an **impedance triangle**.
- Note that an inductive circuit has an impedance triangle in the **first quadrant of complex plane**.

Next

Often, we are given the source voltage.

We take voltage as reference and then find the resulting current.

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{V \angle 0^\circ}{Z \angle \theta} = \frac{V}{Z} \angle -\theta$$

If $v = V_m \sin \omega t$,

$$i = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin \{ \omega t - \tan^{-1} (\omega L) / R \}$$

Click




Click



Next



Example 1

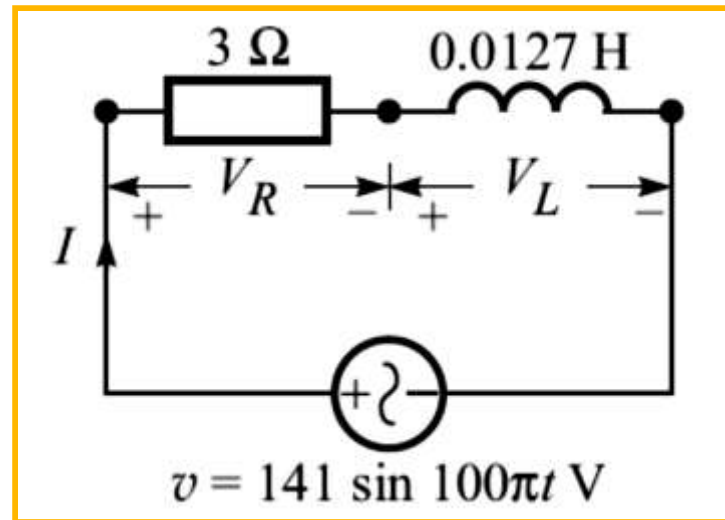

For the series RL circuit shown,

Calculate the rms value of the steady state current and the relative phase angle.

Write the expression for the instantaneous current.

Find the average power dissipated in the circuit.

Determine the power factor.

Draw the phasor diagram.

Next

Solution : The applied voltage can be written as

$$\mathbf{V} = V \angle 0^\circ = \frac{V_m}{\sqrt{2}} \angle 0^\circ = \frac{141}{\sqrt{2}} \angle 0^\circ = 100 \angle 0^\circ \text{ V}$$

Click



The impedance, $\mathbf{Z} = R + j\omega L = 3 + j100\pi \times 0.0127$
 $= 3 + j4 = 5 \angle 53.1^\circ \Omega$

Click



$$\therefore \text{Current, } \mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{100 \angle 0^\circ}{5 \angle 53.1^\circ} = \mathbf{20 \angle -53.1^\circ \text{ A}}$$

$$\therefore i = 20\sqrt{2} \sin(100\pi t - 53.1^\circ)$$
$$= \mathbf{28.28 \sin(100\pi t - 53.1^\circ) \text{ A}}$$

Click



Next



$$P = VI \cos \theta = 100 \times 20 \times \cos 53.1^\circ = \mathbf{1200 \text{ W}}$$

or $P = I^2 R = (20)^2 3 = \mathbf{1200 \text{ W}}$



$$pf = \cos \theta = \cos 53.1^\circ = \mathbf{0.6 \text{ lagging}}$$

or $pf = \frac{P}{VI} = \frac{1200}{100 \times 20} = \mathbf{0.6 \text{ lagging}}$

Click

Click

Click

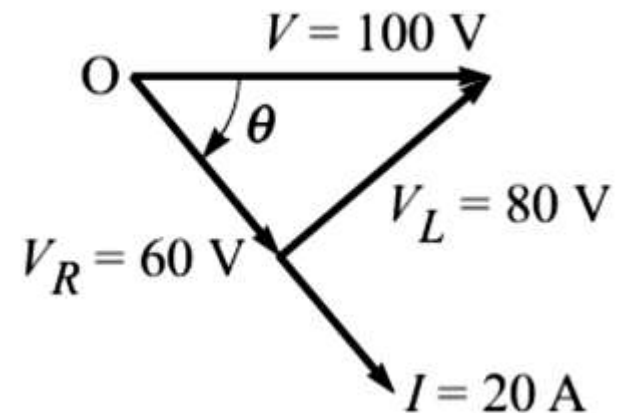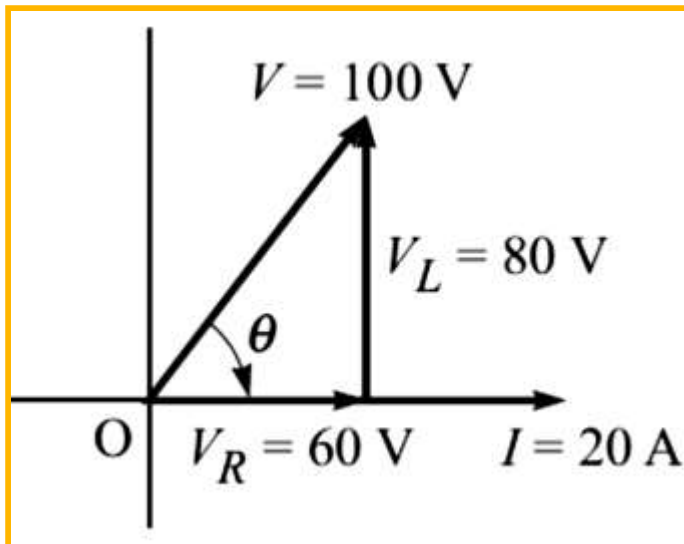


(a) Phasor diagram
(with **I** as ref.)


(a) Phasor diagram
(with **V** as ref.)

Next


Series RC Circuit

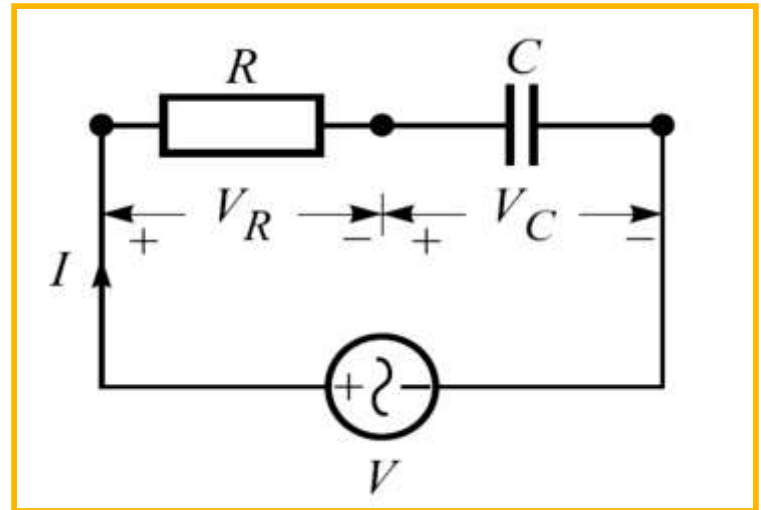


(a) The circuit.

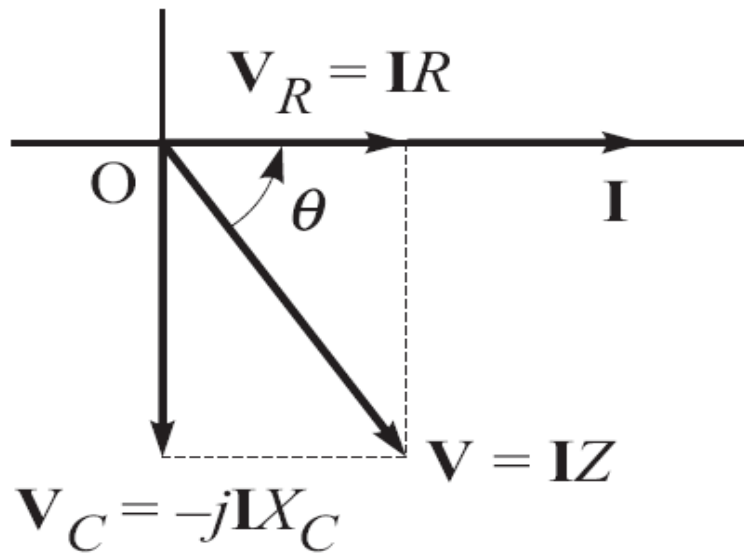

(b) Phasor diagram.

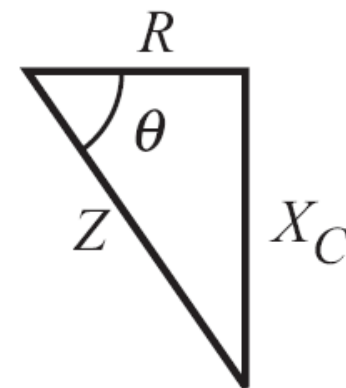

(c) Impedance triangle.

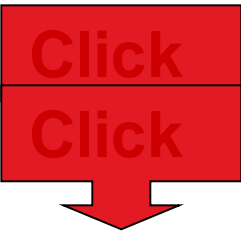

By applying KVL, we get

$$\mathbf{V} = \mathbf{V}_R + \mathbf{V}_C = \mathbf{I}R - j\mathbf{I}X_C = \mathbf{I}(R - jX_C) = \mathbf{I}\left(R - j\frac{1}{\omega C}\right) = \mathbf{I}\mathbf{Z}$$

Since the voltage across a capacitor lags the current by 90° .

- **Note** that $-j$ is associated with X_C

(whereas $+j$ is associated with X_L).

Click

Next

Complex Power

Let the terminal voltage, $\mathbf{V} = V \angle \theta$
and the current, $\mathbf{I} = I \angle \phi$

The average power absorbed, $P = VI \cos(\theta - \phi)$

By using Euler's formula, the above equation

$$P = VI \operatorname{Re}[e^{j(\theta - \phi)}] = \operatorname{Re}[(Ve^{j\theta})(Ie^{-j\phi})]$$

or $P = \operatorname{Re}[\mathbf{VI}^*]$

Next 

We now define the *complex power* as

$$\mathbf{S} = P + jQ = \mathbf{VI}^* = VIe^{j(\theta-\phi)}$$

Note :

- The magnitude VI of \mathbf{S} is the apparent power (VA).
- The angle of \mathbf{S} is the pf angle.
- The real part P of \mathbf{S} is the real power (W).

$$P = VI \cos(\theta - \phi)$$

- The imaginary part Q of \mathbf{S} is reactive power (VAR),

$$Q = VI \sin(\theta - \phi)$$

Next 

Example 2

A current of 0.9 A flows through a series combination of a resistor of $120\ \Omega$ and a capacitor of reactance $250\ \Omega$.

Find the impedance, power factor, supply voltage, voltage across resistor, voltage across capacitor, apparent power, active power and reactive power.

Solution : Let $\mathbf{I} = 0.9 \angle 0^\circ \text{ A}$

$$\mathbf{Z} = 120 - j250 = \mathbf{277.3 \angle -64.4^\circ \Omega}$$

$$pf = \cos \theta = \cos(-64.4^\circ) = \mathbf{0.432 \text{ leading}}$$

$$\mathbf{V} = \mathbf{IZ} = (0.9 \angle 0^\circ)(277.3 \angle -64.4^\circ) = \mathbf{249.6 \angle -64.4^\circ \text{ V}}$$

$$\mathbf{V}_R = \mathbf{IR} = (0.9 \angle 0^\circ) \times 120 = \mathbf{108 \angle 0^\circ \text{ V}}$$

$$\mathbf{V}_C = \mathbf{IX}_C = (0.9 \angle 0^\circ)(250 \angle -90^\circ) = \mathbf{225 \angle -90^\circ \text{ V}}$$

$$P_{app} = \mathbf{VI} = 249.6 \times 0.9 = \mathbf{224.6 \text{ VA}}$$

$$P_a = \mathbf{VI} \cos \theta = 249.6 \times 0.9 \times \cos 64.4^\circ = \mathbf{97.03 \text{ W}}$$

$$P_r = \mathbf{VI} \sin \theta = 249.6 \times 0.9 \times \sin 64.4^\circ = \mathbf{202.55 \text{ VAR}}$$

Click

Click

Click


Click

Click


Click

Next


Series *RLC* Circuit

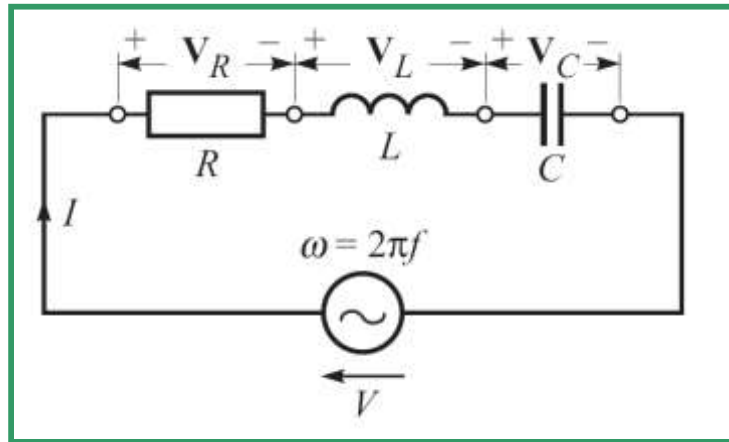

(a) The circuit.

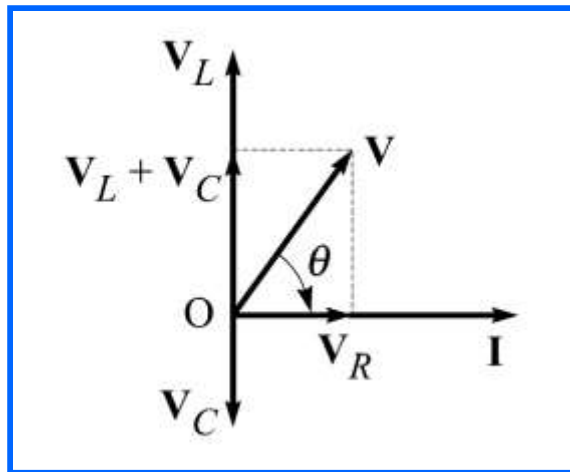

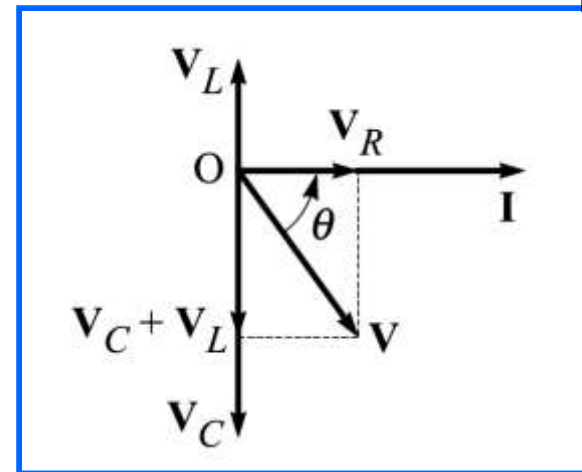(b) Phasor diagram
(when $\omega L > 1/\omega C$)



(c) Phasor diagram
(when $\omega L < 1/\omega C$).



$$\begin{aligned}\mathbf{V} &= \mathbf{V}_R + \mathbf{V}_L + \mathbf{V}_C = \mathbf{I}R + \mathbf{I}(jX_L) + \mathbf{I}(-jX_C) \\ &= \mathbf{I}[R + j(X_L - X_C)] = \mathbf{I}\mathbf{Z}\end{aligned}$$

$$\mathbf{Z} = R + j(X_L - X_C) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$Z = |\mathbf{Z}| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

and $\theta = \tan^{-1} \frac{\omega L - (1/\omega C)}{R}$

Click



Next



There can be following three possibilities :

- (1) **When $\omega L > 1/ \omega C$:** The circuit behaves as an **inductive circuit**.
- (2) **When $\omega L < 1/ \omega C$:** The circuit behaves as a **capacitive circuit**.
- (3) **When $\omega L = 1/ \omega C$:** The circuit behaves as a *purely resistive circuit*. This is a special case, and is called *resonance*.


Next



Example 4

For the circuit shown, calculate (a) the impedance, (b) the current, (c) the phase angle, (d) the voltage across each element, (e) the power factor, (f) the apparent power, and (g) the average power.

Also, draw the phasor diagram.

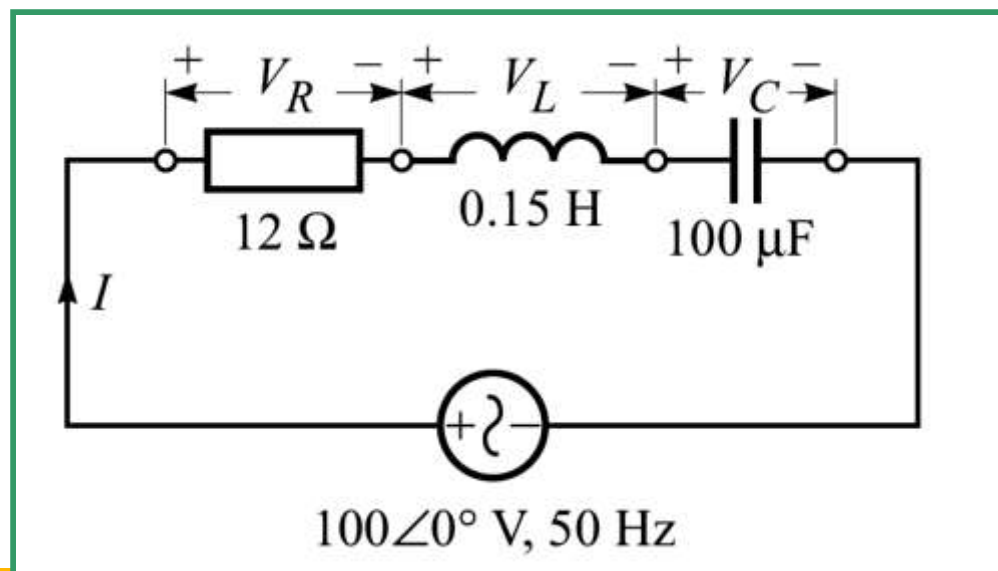

Next

Solution :

$$X_L = \omega L = 2\pi fL = 100\pi \times 0.15 = 47.1 \Omega;$$

$$X_C = 1/\omega C = 1/(100\pi \times 100 \times 10^{-6}) = 31.8 \Omega$$

(a) The impedance,

$$\begin{aligned} \mathbf{Z} &= R + j(X_L - X_C) = 12 + j(47.1 - 31.8) = (12 + j15.3) \Omega \\ &= \mathbf{19.4 \angle 51.9^\circ \Omega} \end{aligned}$$

(b) The current,

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{100 \angle 0^\circ}{19.4 \angle 51.9^\circ} = \mathbf{5.15 \angle -51.9^\circ \text{ A}}$$

(c) The phase angle,

$$\phi = \mathbf{-51.9^\circ}$$

Click

Click

Click

Next

(e) The power factor,


$$pf = \cos 51.9^\circ = \mathbf{0.617 \text{ lagging}}$$

(f) The apparent power,

$$P_{app} = VI = 100 \times 5.15 = \mathbf{515 \text{ VA}}$$

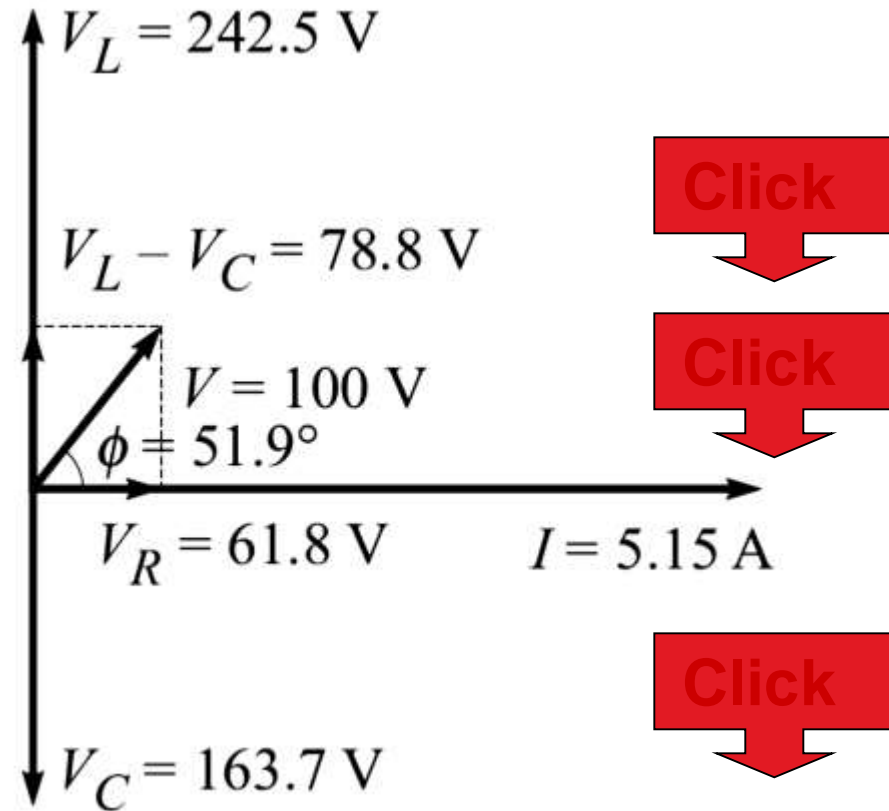(g) The average power,

$$P_{avg} = VI \cos 51.9^\circ = \mathbf{317.75 \text{ W}}$$



Phasor Diagram

Next 

Example 5

A $100\text{-}\Omega$ resistor is connected in series with a choke coil.


When a 440-V , 50-Hz ac voltage is applied to this combination, the voltage across the resistor and the choke coil are 200 V and 300 V , respectively.


Find the power consumed by the choke coil.

Sketch a neat phasor diagram, indicating the current and all voltages.

Solution :

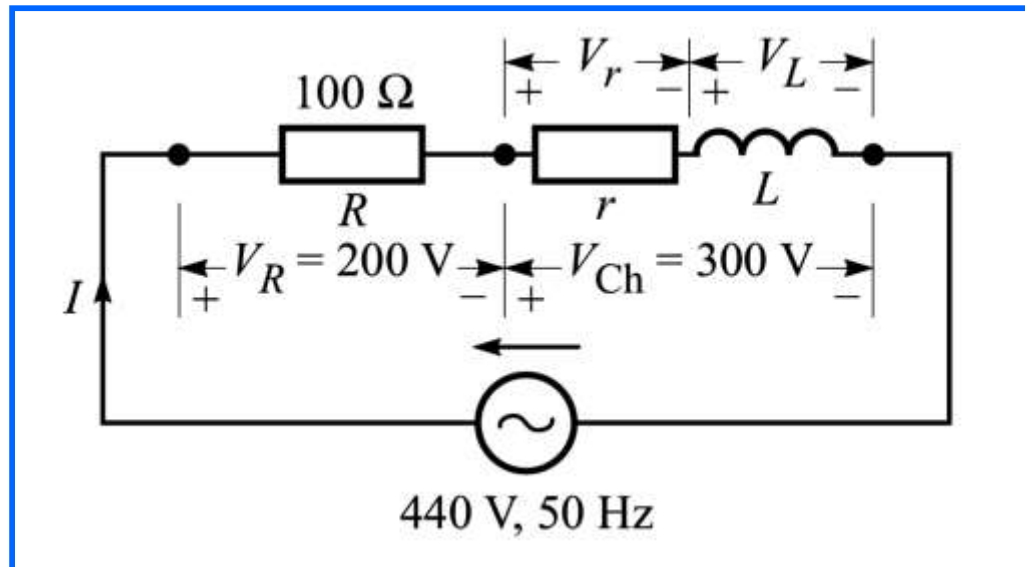- A choke coil has some resistance, say r , and some inductance, say L .
- Because of this resistance r , the voltage V_{Ch} leads the current I by an angle less than 90° (say, angle θ).
- Hence, $\mathbf{V} = \mathbf{V}_R + \mathbf{V}_{\text{Ch}}$.



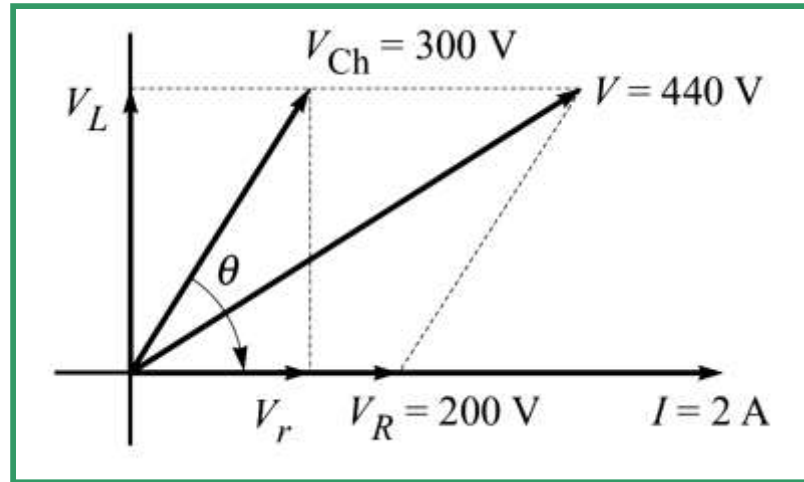

$$V^2 = V_R^2 + V_{Ch}^2 + 2V_R V_{Ch} \cos \theta$$

$$\Rightarrow \cos \theta = \frac{(440)^2 - (200)^2 - (300)^2}{2 \times 200 \times 300} = 0.53$$

Now, $I = \frac{V_R}{R} = \frac{200}{100} = 2\text{ A};$

$$\therefore P = V_{Ch} \times I \times \cos \theta = 300 \times 2 \times 0.53 = \mathbf{318\text{ W}}$$

Click

Click

Click

Next

Review


- **Series *RL* Circuit.**
- **How to Draw Phasor Diagram.**
- **Complex Impedance.**
- **Impedance Triangle.**
- **Series *RC* Circuit.**
- **Complex Power.**
- **Series *RLC* Circuit.**

Next




Out of Syllabus

Parallel RL Circuit

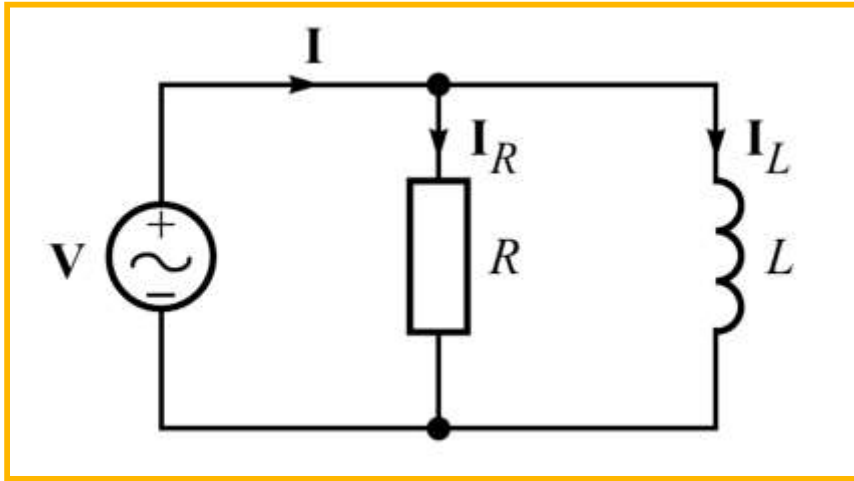

(a) The circuit.

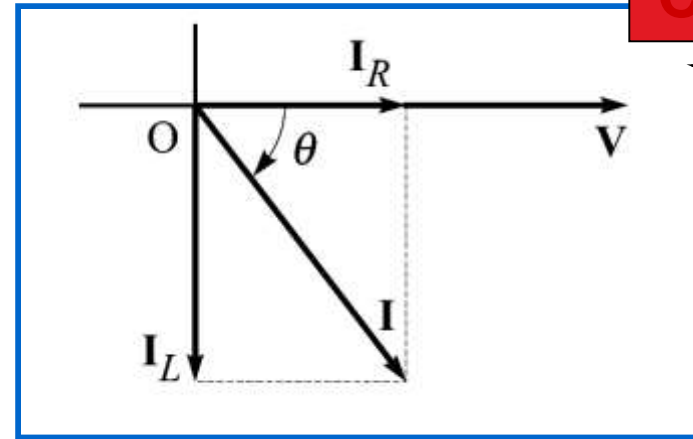

(b) Phasor diagram.

$$\mathbf{I}_R = \frac{\mathbf{V}}{R} \quad \text{and} \quad \mathbf{I}_L = \frac{\mathbf{V}}{jX_L} = \frac{\mathbf{V}}{j\omega L}$$

$$\therefore \mathbf{I} = \mathbf{I}_R + \mathbf{I}_L = \frac{\mathbf{V}}{R} + \frac{\mathbf{V}}{j\omega L} = \mathbf{V} \left(\frac{1}{R} - j \frac{1}{\omega L} \right) = \mathbf{V} \mathbf{Y}$$

Click

Click

Next

Y is the complex admittance of the parallel RL circuit,


$$\mathbf{Y} = \frac{1}{R} + \frac{1}{j\omega L} = \frac{1}{R} - j\frac{1}{\omega L}$$

$$\mathbf{Y} = G + jB = (\text{conductance}) + j(\text{susceptance})$$


For parallel RL circuit, $G = 1/R$ and $B = -1/\omega L$

Next 

Parallel RC Circuit

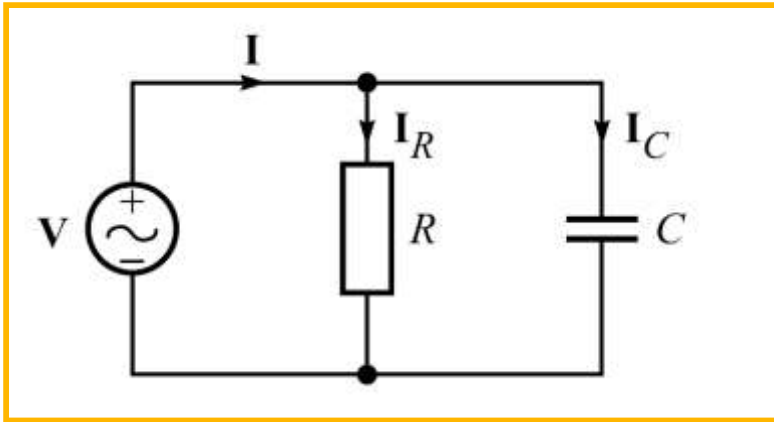

(a) The circuit.

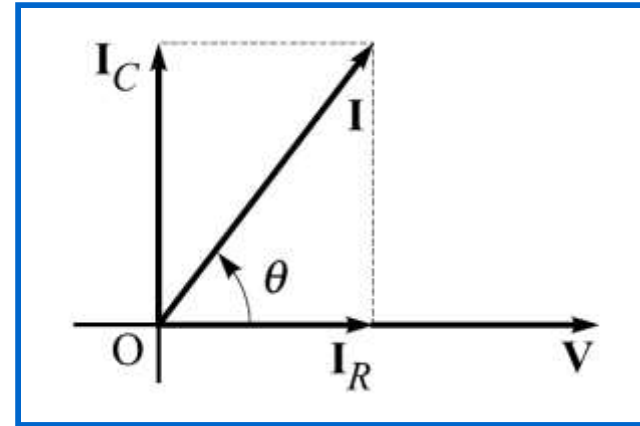

(b) Phasor diagram.

$$\mathbf{I}_R = \frac{\mathbf{V}}{R} \quad \text{and} \quad \mathbf{I}_C = \frac{\mathbf{V}}{-jX_C} = \frac{\mathbf{V}}{-j(1/\omega C)} = \mathbf{V}(j\omega C)$$

$$\mathbf{I} = \mathbf{I}_R + \mathbf{I}_C = \frac{\mathbf{V}}{R} + \mathbf{V}(j\omega C) = \mathbf{V} \left(\frac{1}{R} + j\omega C \right) = \mathbf{V}\mathbf{Y}$$

Click

Click

Next

The complex admittance,

$$\mathbf{Y} = (G + jB) = \left(\frac{1}{R} + j\omega C \right)$$



Example 3

When a two-element parallel circuit is connected across an ac source of frequency 50 Hz, it offers an impedance $Z = (10 - j10) \Omega$. Determine the values of the two elements.

Solution : The nature of the impedance indicates that the circuit is capacitive. We find the admittance of the circuit,

Next 

$$\mathbf{Y} = (G + jB) = \frac{1}{\mathbf{Z}} = \frac{1}{10 - j10} = (0.05 + j0.05) \text{ S}$$




$$\therefore G = 0.05 \text{ S} \Rightarrow R = \frac{1}{G} = \frac{1}{0.05} = \mathbf{20 \Omega}$$


$$\text{and } B = 0.05 \text{ S} \Rightarrow C = \frac{B}{\omega} = \frac{0.05}{2\pi f} = \mathbf{159 \mu\text{F}}$$



Parallel RLC Circuit

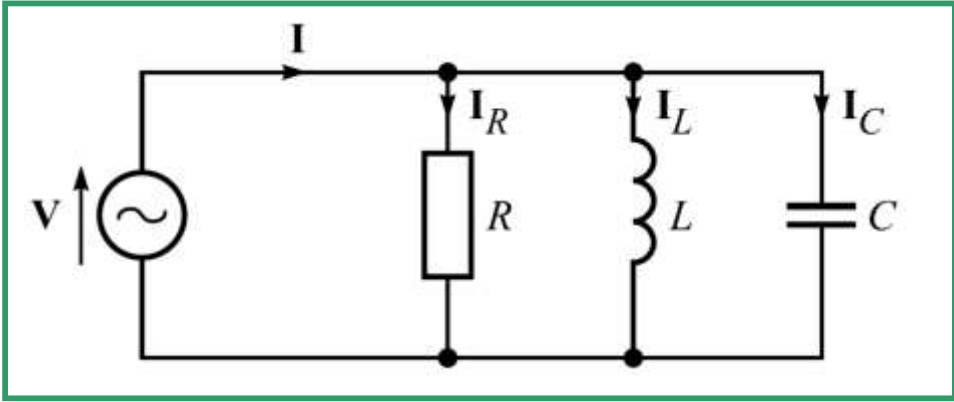


(a) The circuit.

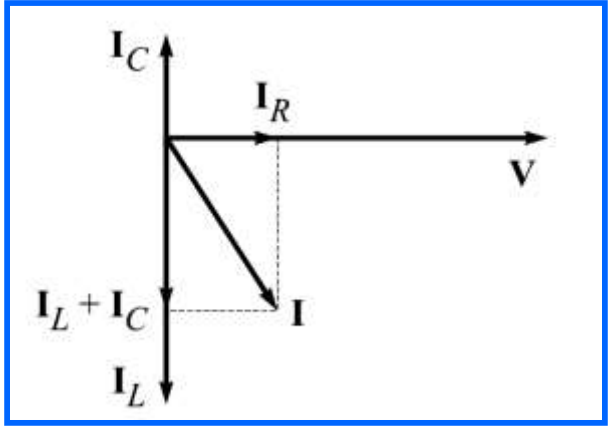

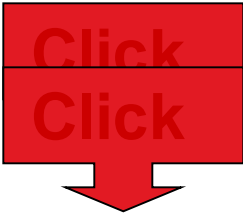(b) Phasor diagram.

$$\begin{aligned} \mathbf{I} &= \mathbf{I}_R + \mathbf{I}_L + \mathbf{I}_C = \frac{\mathbf{V}}{R} + \frac{\mathbf{V}}{jX_L} + \frac{\mathbf{V}}{-jX_C} \\ &= \mathbf{V}G + \mathbf{V}(-jY_L) + \mathbf{V}(jY_C) \end{aligned}$$

or $\mathbf{I} = \mathbf{V}[G + j(Y_C - Y_L)] = \mathbf{V}\mathbf{Y}$



Obviously,

$$G = \frac{1}{R}; \quad Y_L = \frac{1}{X_L} = \frac{1}{\omega L} \quad \text{and} \quad Y_C = \frac{1}{X_C} = \frac{\omega C}{1} = \omega C$$

Note that $+j$ is associated with Y_C (and not with X_L) and $-j$ with Y_L .

Next 